

CSE460

Lab Assignment 3

Submitted by: Masiat Hasin Rodoshi

ID: 19201089

Section: 4

Date: 16.11.2022

Problem statement: A sequential circuit has two inputs, **w1** and **w2**, and an output, **z**. Its function is to compare the input sequences on the two inputs. If **w1 = w2** during any **four** consecutive clock cycles, the circuit produces **z = 1**; otherwise, **z = 0**.

Code implementation:

```
module lab3_19201089(z,w1,w2,clk,reset,next_state,current_state);
input clk, reset, w1, w2;
output reg z;
output reg [1:0] current_state, next_state;
parameter [1:0] A=2'b00, B =2'b01, C =2'b10, D =2'b11;
    always @(posedge clk, posedge reset)
        if (reset == 1)
            begin
                current_state = A;
                next_state = A;
            end
        else
            begin
                current_state = next_state;
                case(current_state)
                    A: if ((w1 == 0 && w2 == 1) || (w1 == 1 && w2 == 0))
                        begin
                            z <= 0;
                            next_state <= A;
                        end
                end
            end
        else
            begin
```

```
z <= 0;  
next_state <= B;  
end
```

```
B: if ((w1 == 0 && w2 == 0) || (w1 == 1 && w2 == 1))
```

```
begin  
z <= 0;  
next_state <= C;  
end
```

```
else
```

```
begin  
z <= 0;  
next_state <= A;  
end
```

```
C: if ((w1 == 0 && w2 == 0) || (w1 == 1 && w2 == 1))
```

```
begin  
z <= 0;  
next_state <= D;  
end
```

```
else
```

```
begin  
z <= 0;  
next_state <= A;  
end
```

```
D: if ((w1 == 0 && w2 == 0) || (w1 == 1 && w2 == 1))
```

```


begin
    z <= 1;
    next_state <= D;
end
else
begin
    z <= 0;
    next_state <= A;
end
endcase
end
endmodule

```

Compilation report:

| Compilation Report - Flow Summary | | lab3_19201089.vwf | Simulation Report - Simulation Waveforms |
|-----------------------------------|---|-------------------|--|
| Flow Summary | | | |
| Flow Status | Successful - Wed Nov 16 20:10:35 2022 | | |
| Quartus II Version | 8.1 Build 163 10/28/2008 SJ Web Edition | | |
| Revision Name | lab3_19201089 | | |
| Top-level Entity Name | lab3_19201089 | | |
| Family | FLEX10KE | | |
| Met timing requirements | Yes | | |
| Total logic elements | 7 / 1,728 (< 1 %) | | |
| Total pins | 9 / 102 (9 %) | | |
| Total memory bits | 0 / 24,576 (0 %) | | |
| Total PLLs | 0 | | |
| Device | EPF10K30ETC144-1 | | |
| Timing Models | Final | | |

Simulation report:

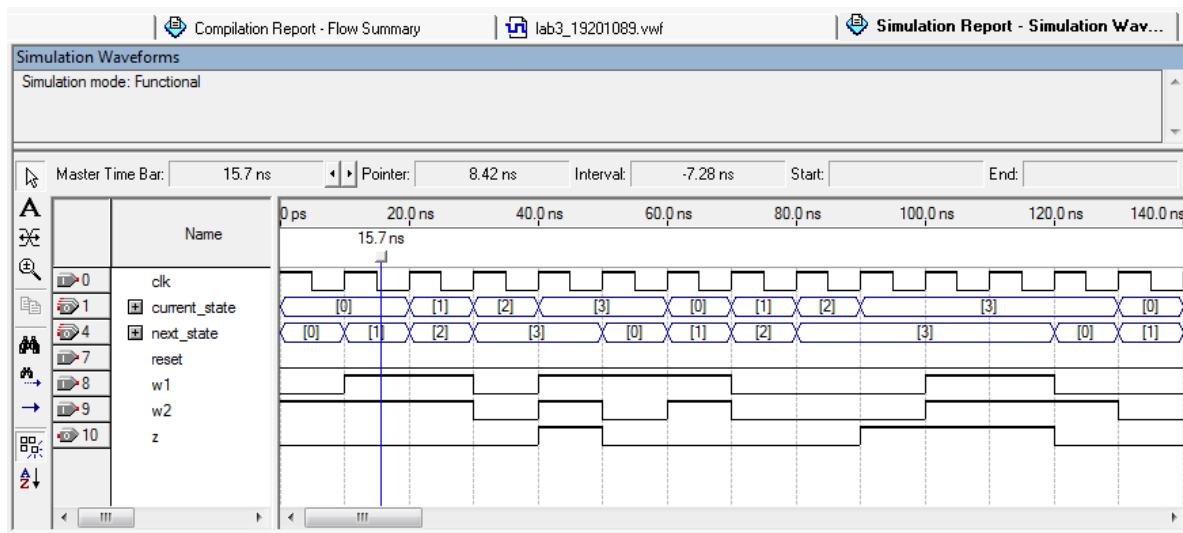

Discussion:

According to the question, we are to design a finite state machine that takes two inputs, w1 and w2 and gives the output z. If w1 = w2 for any four consecutive clock cycles, then z = 1, otherwise z = 0.


For example:

```

w1 : 0 1 1 0 1 1 1 0 0 0 1 1 0
w2 : 1 1 1 0 1 0 1 0 0 0 1 1 1
z  : 0 0 0 0 1 0 0 0 0 1 1 1 0

```

 This is a mealy type machine because the output is generated in the same clock cycle where the conditions have been met. We can see the FSM for this problem below.



Since the length of the accepted string is four, we have four states and we go to the next state when $w1 = w2$ and $w1, w2$ can be either 0 or 1. State D is the final accepting state where $z = 1$ and we will remain here as long as $w1 = w2$. However, in any state, if we find $w1 \neq w2$, we will return to state A which is the starting state and try again to find a sequence that meets the requirements.

In the timing diagram, at time = 40ns, we find $z = 1$ because in this clock cycle and the previous three clock cycles, the values of $w1$ were equal to $w2$. Similarly, from time 90-110ns, $z=1$ because the consecutive four values including their respective clock cycles saw $w1 = w2$. Therefore, we can say that the simulation is accurate.